

Introduction To Microelectronic Circuits
Assignment 1

Amplifier Biasing:

Choose any three of the following 5 biasing problems:

1. Bias a CS NMOS amplifier in a 1 μm CMOS process described by $\mu_n C_{OX} = 0.1 \text{ mA/V}$, $V_t = 0.5 \text{ V}$ and $\lambda'_n = 2 \times 10^{-7} \text{ m/V}$ such that its output is set at 1.65 V. Assume a 3.3 V supply level and that the source terminal is set at 0 V. Ensure that the device is operating in its saturation region. Verify your result using SPICE.
2. Bias a CS PMOS amplifier in a 1 μm CMOS process described by $\mu_p C_{OX} = 0.05 \text{ mA/V}$, $V_t = -0.6 \text{ V}$ and $\lambda'_p = 5 \times 10^{-7} \text{ m/V}$ such that its output is set at 1.65 V. Assume a 3.3 V supply level and that the source terminal is set at 3.3 V. Ensure that the device is operating in its saturation region. Verify your result using SPICE.
3. Bias a CG NMOS amplifier in a 1 μm CMOS process described by $\mu_n C_{OX} = 0.1 \text{ mA/V}$, $V_t = 0.5 \text{ V}$ and $\lambda'_n = 2 \times 10^{-7} \text{ m/V}$ such that its output is set at 2.2 V. Assume a 3.3 V supply level and that the source terminal is set at 1.2 V. Ensure that the device is operating in its saturation region. Verify your result using SPICE.
4. Bias a CB npn amplifier in a bipolar process described by $V_A = 100 \text{ V}$ and $I_S = 1 \times 10^{-15} \text{ A}$ such that its output is set at 5 V. Assume a $\pm 12 \text{ V}$ split supply level and that the base terminal is set at 0 V. Ensure that the device is operating in its active region. Verify your result using SPICE.
5. Bias a CD PMOS amplifier in a 1 μm CMOS process described by $\mu_p C_{OX} = 0.05 \text{ mA/V}$, $V_t = -0.6 \text{ V}$ and $\lambda'_p = 5 \times 10^{-7} \text{ m/V}$ such that its output is set at 1.65 V. Assume a 3.3 V supply level. Ensure that the device is operating in its saturation region. Verify your result using SPICE.